

1 D4 - TEKKOM B

COUNTER



Nama : Septian Bagus Jumentoro
Kelas : 1 – D4 Teknik Komputer B
NRP : 3221600039
Dosen : Reni Soelistijorini B.Eng., MT.
Mata Kuliah : Praktikum Rangkaian Logika
Hari,Tgl. Praktikum : Jumat, 27 Mei 2022

1. Tujuan

Dapat menjelaskan rangkaian pembagi clock. Dapat membuat rangkaian Counter modulus 10k.

2. Teori

Clock Divider

Frekuensi dan periode dari Xilinx Spartan 3 adalah 24-bit counter dengan clock sebesar 50MHz. Counter dapat digunakan untuk membagi frekuensi f dari clock, dimana frekuensi output $q(i)$ adalah $f_i = f/2^{i+1}$. Tabel 2.1 menyatakan pembagian frekuensi.

Tabel 8.1 Clock divide frequencies

q(i)	Frekuensi (Hz)	Periode(ms)
i	50000000.00	0.00002
0	25000000.00	0.00004
1	12500000.00	0.00008
2	6250000.00	0.00016
3	3125000.00	0.00032
4	1562500.00	0.00064
5	781250.00	0.00128
6	390625.00	0.00256
7	195312.50	0.00512
8	97656.25	0.01024
9	48828.13	0.02048
10	24414.06	0.04096
11	12207.03	0.08192
12	6103.52	0.16384
13	3051.76	0.32768
14	1525.88	0.65536
15	762.94	1.31072
16	381.47	2.62144
17	190.73	5.24288
18	95.37	10.48576
19	47.68	20.97152
20	23.84	41.94304
21	11.92	83.88608
22	5.96	167.77216
23	2.98	335.54432

Counter

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Counter is
    generic(N : integer :=8);
    Port ( clk : in STD_LOGIC;
          clr : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (N-1 downto 0));
end Counter;

architecture Behavioral of Counter is
    signal count : std_logic_vector (N-1 downto 0);
begin
    process (clk, clr)
    begin
        if clr = '1' then
            count <= (others => '0');
        elsif clk'event and clk='1' then
            count <= count + 1;
        end if;
        q <= count;
    end process;
end Behavioral;

```

```

-- Example 4
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity clkdiv is
    port(
        mclk : in STD_LOGIC;
        clr : in STD_LOGIC;
        clk25 : out STD_LOGIC;
        clk190 : out STD_LOGIC;
        clk3 : out STD_LOGIC
    );
end clkdiv;
architecture clkdiv of clkdiv is
    signal q : STD_LOGIC_VECTOR(23 downto 0);
begin
    -- clock divider
    process(mclk, clr)
    begin

```

```

        if clr = '1' then
            q <= X"000000";
        elsif mclk'event and mclk = '1' then
            q <= q + 1;
        end if;
    end process;

    clk25 <= q(0);           -- 25Mhz
    clk190 <= q(17);        -- 190Hz
    clk3 <= q(23);          -- 3Hz

end clkdiv;

```

Scrip 8.1 Clock Divider

Pada skrip 8.1 adalah contoh 24-bit counter yang mempunyai 3 output, yaitu 25Mhz clock (clk25), clock 190Hz (clk190), dan clock 3Hz (clk3). Untuk memodifikasi component *clkdiv* untuk bisa menghasilkan output frekuensi yang berbeda dengan menggunakan tabel 8.1.


3. Peralatan

1. PC yang sudah terinstal ISE 13.1
2. Xilinx Spartan 3
3. Downloader JTAG USB
4. Power Supply 5 volt

4. Langkah Percobaan

Pada percobaan ini akan mendisain counter 0-9999. Masukan rangkaian ini adalah mclk 50Mhz dan button Reset. Keluaran di seven segmen(a_to_g) dan enable(an(3:0)).

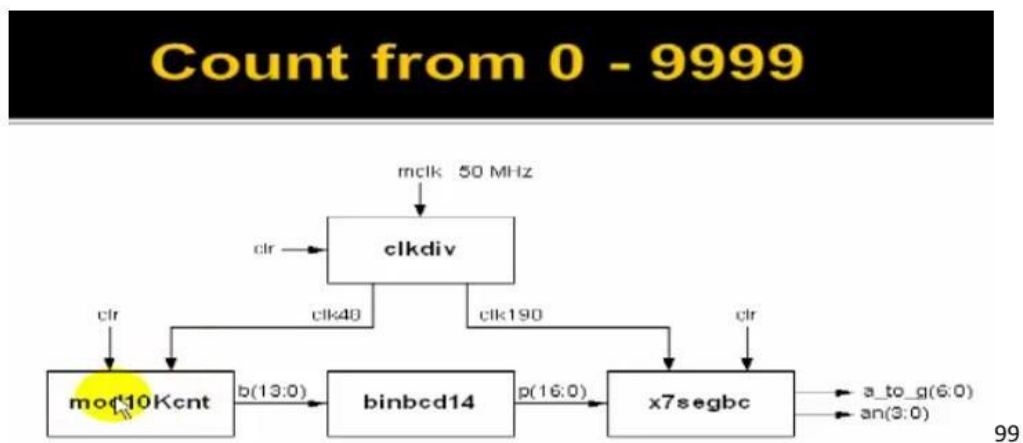1. Buatlah *new project* dengan nama **Lab8**.
2. Tambahkan program VHDL dibawah ini.



Clock Divider

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Clockdiv is
    port (    Clk25Mhz : in STD_LOGIC;
            Clk : out STD_LOGIC);
    end Clockdiv;

architecture Behavior of Clockdiv is
    constant max : integer := 25000000;
    constant half : integer := max/2;
    signal count : integer range 0 to max;
begin
    process
    begin
        wait until Clk25Mhz' EVENT and Clk25Mhz = '1';
        if count < max then
            count <= count + 1;
        else
            count <= 0;
        end if;

        if count < half then
            Clk <= '0';
        else
            Clk <= '1';
        end if;
    end process;
end Behavior;
```

Clock divider 48Hz dan 190Hz

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity clkdv is
    Port ( nclk : in STD_LOGIC;
            clr : in STD_LOGIC;
            clk190 : out STD_LOGIC;
            clk48 : out STD_LOGIC);
    end clkdv;

architecture Behavioral of clkdv is
    signal q:std_logic_vector(23 downto 0);
begin
    -- clock divider
    c
```

```
    process(nclk, clr)
    begin
        if clr = '1' then
            q <= x"000000"; -- format hexadecimal
        elsif nclk'event and nclk = '1' then
            q <= q + 1;
        end if;
        clk48 <= q(19);
        clk190 <= q(17);
    end process;
end Behavioral;
```

Counter modulus 10K.

```

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mod10kcnt is
    Port ( clr : in STD_LOGIC;
          clk : in STD_LOGIC;
          q : out STD_LOGIC_VECTOR (13 downto 0));
end mod10kcnt;

architecture Behavioral of mod10kcnt is
    signal count : STD_LOGIC_VECTOR (13 downto 0);
begin
    -- modulo 10k
    process(clk, clr)
    begin
        if clr = '1' then
            count <= (others => '0');
        elsif clk'event and clk = '1' then
            if conv_integer(count) = 9999 then
                count <= (others => '0');
            else
                count <= count + 1;
            end if;
        end if;
    end process;
    q <= count;
end Behavioral;

```

Biner 14 bit to BCD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity binBCD14 is
    Port ( b : in STD_LOGIC_VECTOR (13 downto 0);
          p : out STD_LOGIC_VECTOR (16 downto 0));

```

```

end binBCD14;

architecture Behavioral of binBCD14 is
begin
    process(b)
        variable z : STD_LOGIC_VECTOR (32 downto 0);
    begin
        for i in 0 to 32 loop
            z(i) := '0';
        end loop;

        z(16 downto 3) := b;
        for i in 0 to 10 loop
            if z(17 downto 14) > 4 then
                z(17 downto 14) := z(17 downto 14) + 3;
            end if;
            if z(21 downto 18) > 4 then
                z(21 downto 18) := z(21 downto 18) + 3;
            end if;
            if z(25 downto 22) > 4 then
                z(25 downto 22) := z(25 downto 22) + 3;
            end if;
            if z(29 downto 26) > 4 then
                z(29 downto 26) := z(29 downto 26) + 3;
            end if;
            z(32 downto 1) := z(31 downto 0);
        end loop;
        p <= z(30 downto 14);
    end process;
end Behavioral;

```

x7segbc

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity x7segbc is
    port( x      : in std_logic_vector (15 downto 0);
          clk     : in std_logic;
          clr     : in std_logic;
          a_to_g  : out std_logic_vector (6 downto 0);
          an      : out std_logic_vector (3 downto 0);
          dp      : out std_logic
    );
end x7segbc;
```

cii

```
architecture Behavioral of x7segbc is
    signal s : std_logic_vector (1 downto 0);
    signal digit : std_logic_vector (3 downto 0);
    signal aen : std_logic_vector (3 downto 0);
begin
    dp <= '1';
    -- set aen(3 downto 0) for leading blanks
    aen(3) <= x(15) or x(14) or x(13) or x(12);
    aen(2) <= x(15) or x(14) or x(13) or x(12)
        or x(11) or x(10) or x(9) or x(8);
    aen(1) <= x(15) or x(14) or x(13) or x(12)
        or x(11) or x(10) or x(9) or x(8)
        or x(7) or x(6) or x(5) or x(4);
    aen(0) <= '1';

    -- Quad 4-to-1 MUX: mux44
    process(s,x)
    begin
        case s is
            when "00" => digit <= x(3 downto 0);
            when "01" => digit <= x(7 downto 4);
            when "10" => digit <= x(11 downto 8);
            when others => digit <= x(15 downto 12);
        end case;
    end process;

    -- 7-segment decoder: hex7seg
    process(digit)
    begin
        case digit is
            when x"0" => a_to_g <= "0000001"; -- 0
            when x"1" => a_to_g <= "1001111"; -- 1
            when x"2" => a_to_g <= "0010010"; -- 2
            when x"3" => a_to_g <= "0000110"; -- 3
            when x"4" => a_to_g <= "1001100"; -- 4
            when x"5" => a_to_g <= "0100100"; -- 5
            when x"6" => a_to_g <= "0100000"; -- 6
            when x"7" => a_to_g <= "0001111"; -- 7
            when x"8" => a_to_g <= "0000000"; -- 8
            when x"9" => a_to_g <= "0000100"; -- 9
            when x"A" => a_to_g <= "0001000"; -- a
            when x"B" => a_to_g <= "1100000"; -- b
            when x"C" => a_to_g <= "0110001"; -- c
            when x"D" => a_to_g <= "1000010"; -- d
        end case;
    end process;
end;
```

```

        when x"E" => a_to_g <= "0110000"; --e
        when others => a_to_g <= "0111000"; --f
    end case;
end process;

-- Digit select: ancode
process(s,aen)
begin
    an <= "1111";
    if aen(conv_integer(s))='1' then
        an(conv_integer(s))<='0';
    end if;
end process;

-- 2 bit counter
process(cclk, clr)
begin
    if clr='1' then
        s <= "00";
    elsif cclk'event and cclk='1' then
        s <= s + 1;
    end if;
end process;
end Behavioral ;

```

Mod10Kcnt_top

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity mod10Kcnt_top is
    port( nclk : in std_logic;
          btn   : in std_logic;
          a_to_g : out std_logic_vector(6 downto 0);
          an     : out std_logic_vector(3 downto 0);
          dp     : out std_logic
    );
end entity;

```



```

    );
end mod10Kcnt_top;

architecture Behavioral of mod10Kcnt_top is
    component clkdiv is
        port( nclk : in std_logic;
              clr  : in std_logic;
              clk190: out std_logic;
              clk48: out std_logic
            );
    end component;
    component mod10kcnt is
        port(      clr : in STD_LOGIC;
                clk  : in STD_LOGIC;
                q    : out STD_LOGIC_VECTOR (13 downto 0)
            );
    end component;
    component btnbcd14 is
        Port (      b : in STD_LOGIC_VECTOR (13 downto 0);
                p : out STD_LOGIC_VECTOR (16 downto 0));
    end component;
    component x7segbc is
        port( x      : in std_logic_vector (15 downto 0);
              cclk   : in std_logic;
              clr     : in std_logic;
              a_to_g  : out std_logic_vector (6 downto 0);
              an      : out std_logic_vector (3 downto 0);
              dp      : out std_logic
            );
    end component;

    signal b : std_logic_vector (13 downto 0);
    signal p : std_logic_vector (16 downto 0);
    signal clr, clk48, clk190 : std_logic;

begin
    clr <= btn;

    u1: clkdiv port map(
        nclk => nclk,
        clr  => clr,
        clk190 => clk190,
        clk48 => clk48
    );

```

```


    u2: mod10kcnt port map(
        clr => clr,
        clk => clk48,
        q => b
    );
    u3: btnbcd14 port map(
        b => b,
        p => p
    );
    u4: x7segbc port map(
        x      => p(15 downto 0),
        cclk   => clk190,
        clr     => clr,
        a_to_g  => a_to_g,
        an      => an,
        dp      => dp
    );

end Behavioral ;

```

3. Pastikan program **Mod10Kcnt_top** menjadi top module.
4. Lakukan sintesis, sehingga menghasilkan RTL schematics seperti dibawah ini.

Hasil RTL Schematics

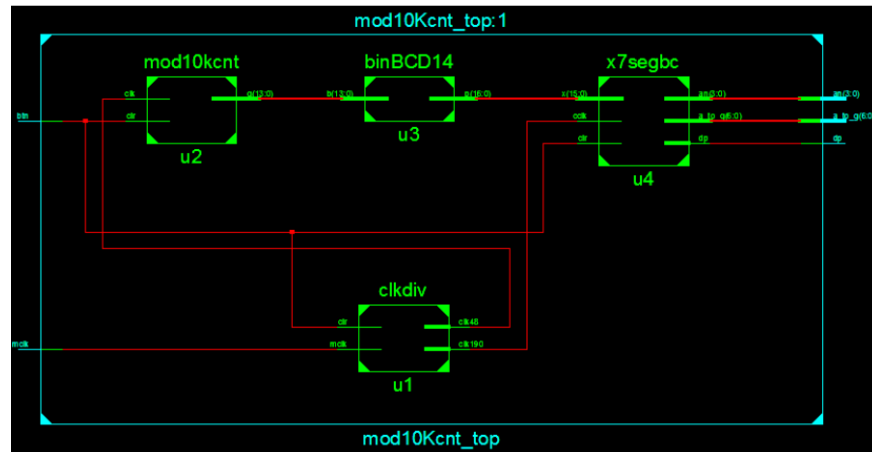

5. Upload program ke board spartan, setelah sukses demokan hasilnya ke dosen pengampu

5. Latihan

Buatlah program stop watch, dengan menggunakavni push button untuk tombol start, pause, reset.

6. Hasil Percobaan

a. Langkah Percobaan

Pendefinisian Pin

```

1 net btn(0) LOC = M13;
2 net btn(1) LOC = M14;
3
4 NET a_to_g(0) LOC = N16;
5 NET a_to_g(1) LOC = F13;
6 NET a_to_g(2) LOC = R16;
7 NET a_to_g(3) LOC = P15;
8 NET a_to_g(4) LOC = N15;
9 NET a_to_g(5) LOC = G13;
10 NET a_to_g(6) LOC = E14;
11
12 net an(0) LOC = D14;
13 net an(1) LOC = G14;
14 net an(2) LOC = F14;
15 net an(3) LOC = E13;
16
17 NET dp LOC = P16;
```

RTL Skematik


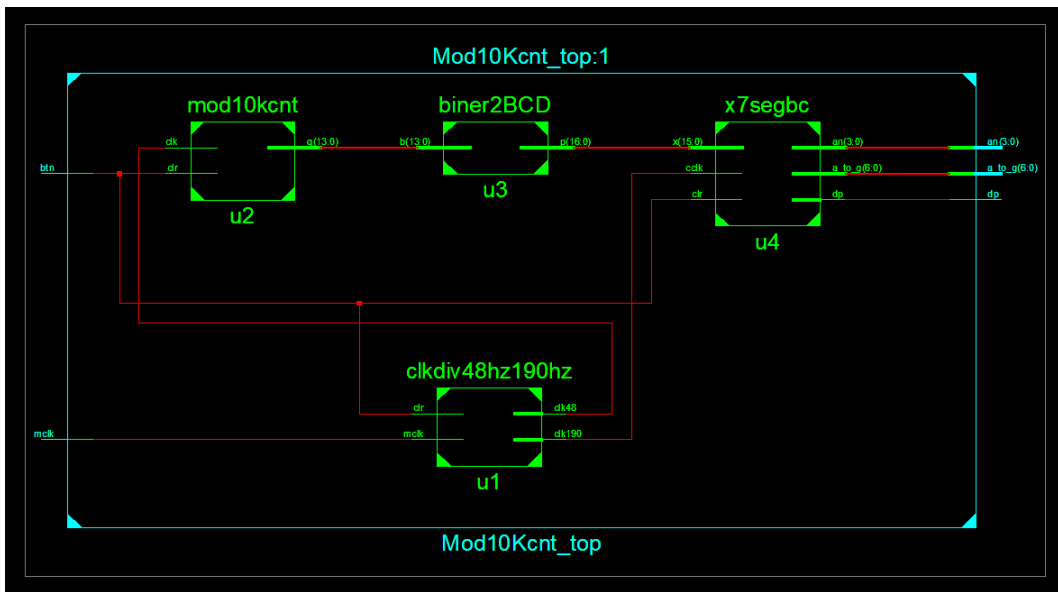


Foto Percobaan pada FPGA Board

 

Gambar Output 6645 pada 7 Segment Display



Gambar Output 7688 pada 7 Segment Display

b. Mini Project

Kode program

Clock Divider

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity clkdiv is
Port (mclk : in  STD_LOGIC;
      clr : in STD_LOGIC;
      clk190 : out STD_LOGIC;
      clk48 : out STD_LOGIC);
end clkdiv;

architecture Behavioral of clkdiv is
signal q:std_logic_vector(23 downto 0);
begin
    process(mclk, clr)
    begin
        if clr = '1' then
            q <= x"000000"; --format hexadecimal
        elsif mclk' event and mclk = '1' then
            q <= q + 1;
        end if;
        clk48 <= q(19); clk190 <= q(17);
    end process;
end Behavioral ;
```

Modulus

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity mod10kcnt is
Port (clr : in STD_LOGIC;
      clk : in STD_LOGIC;
      start : in STD_LOGIC;
      pause : in STD_LOGIC;
      q : out STD_LOGIC_VECTOR (13 downto 0));
end mod10kcnt;

architecture Behavioral of mod10kcnt is
signal count:STD_LOGIC_VECTOR (13 downto 0);
signal flagrun:std_logic;
begin
    -- modul o 10k
    process(clk,clr,start,pause)
    begin
        -- reset and counter
        if clr = '1' then
            count <= (others => '0');
        elsif clk' event and clk = '1' then
            if start = '1' and pause = '0' then
                flagrun <= '1';
            elsif start = '0' and pause = '1' then
                flagrun <= '0';
            end if;
            if conv_integer (count) = 9999 then
                count <= (others => '0');
            elsif flagrun = '1' then
```

```

                                count <= count + 1;
                                end if;
                                end if;
                                end process;
                                q <= count ;
end Behavioral ;

```

Binary to BCD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity binBCD14 is
    Port (b : in STD_LOGIC_VECTOR (13 downto 0);
          p : out STD_LOGIC_VECTOR (16 downto 0));
end binBCD14;
architecture Behavioral of binBCD14 is
begin
    process(b)
        variable z : STD_LOGIC_VECTOR (32 downto 0);
    begin
        for i in 0 to 32 loop
            z (i) := '0';
        end loop;
        z (16 downto 3) := b;
        for i in 0 to 10 loop
            if z (17 downto 14) > 4 then
                z (17 downto 14) := z (17 downto 14) + 3;
            end if;
            if z (21 downto 18) > 4 then
                z (21 downto 18) := z (21 downto 18) + 3;
            end if;
            if z (25 downto 22) > 4 then
                z (25 downto 22) := z (25 downto 22) + 3;
            end if;
            if z (29 downto 26) > 4 then
                z (29 downto 26) := z (29 downto 26) + 3;
            end if;
            z (32 downto 1) := z (31 downto 0);
        end loop;
        p <= z (30 downto 14);
    end process;
end Behavioral ;

```

Decoder 7 Segment

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity x7segbc is
    port(x: in std_logic_vector (15 downto 0); cclk : in std_logic ; clr
          : in std_logic ;
          a_to_g : out std_logic_vector (6 downto 0); an : out std_logic_vector (3
downto 0); dp: out std_logic);
end x7segbc ;

architecture Behavioral of x7segbc is
    signal s : std_logic_vector (1 downto 0); signal digit : std_logic_vector (3
downto 0); signal aen : std_logic_vector (3 downto 0);
begin
    dp <= '1' ;
    --set aen( 3  downto 0)    f or l eadi ng bl anks
    aen(3) <= x(15) or x(14) or x(13) or x(12);
    aen(2) <= x(15) or x(14) or x(13) or x(12) or x(11) or x(10) or x(9) or
x(8);
    aen(1) <= x(15) or x(14) or x(13) or x(12) or x(11) or  x(10) or  x(9) or
x(8) or x(7) or x(6) or x(5) or x(4);
    aen(0) <= '1' ;

    --      Quad   4- t o- 1      MUX:
    process(s ,x)
    begin
        case  s is
            when  "00" => digit <= x(3  downto 0);
            when  "01" => digit <= x(7  downto 4);
            when  "10" => digit <= x(11 downto 8);
            when  others => digit <= x(15 downto 12);
        end case;
    end process;

    --      7- segment   decoder :      hex7seg
    process(digit) begin
        case digit    is
            when  x"0"  =>      a_to_g <=      "0000001" ;  -- 0
            when  x"1"  =>      a_to_g <=      "1001111" ;  -- 1
            when  x"2"  =>      a_to_g <=      "0010010" ;  -- 2
            when  x"3"  =>      a_to_g <=      "0000110" ;  -- 3
            when  x"4"  =>      a_to_g <=      "1001100" ;  -- 4
            when  x"5"  =>      a_to_g <=      "0100100" ;  -- 5
            when  x"6"  =>      a_to_g <=      "0100000" ;  -- 6
            when  x"7"  =>      a_to_g <=      "0001111" ;  -- 7
            when  x"8"  =>      a_to_g <=      "0000000" ;  -- 8
            when  x"9"  =>      a_to_g <=      "0000100" ;  -- 9
            when  x"A"  =>      a_to_g <=      "0001000" ;  -- a
            when  x"B"  =>      a_to_g <=      "1100000" ;  -- b
            when  x"C"  =>      a_to_g <=      "0110001" ;  -- c
            when  x"D"  =>      a_to_g <=      "1000010" ;  -- d
            when  x"E" => a_to_g  <= "0110000" ;  -- e
            when  others => a_to_g <= "0111000" ;  -- f
        end case;
    end process;
```

```

-- Di gi t sel ect : ancode
process(s ,aen)
begin
    beginan <= "1111" ;
    if aen(conv_integer (s ))='1'then
        an(conv_integer (s ))<='0' ;
    end if;
end process;

-- 2 bi t count er
process(cclk, clr)
begin
    if clr ='1'    then
        s <= "00" ;
    elsif cclk' event and  cclk='1'    then
        s <= s + 1;
    end if;
end process;
end Behavioral ;

```

Top Modul

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mod10kcnt_top is
port( mclk : in std_logic;
      btn : in std_logic_vector(2 downto 0);
      a_to_g : out std_logic_vector(6 downto 0);
      an : out std_logic_vector(3 downto 0);
      dp : out std_logic
    );
end mod10kcnt_top;

architecture Behavioral of mod10kcnt_top is
    component clkdiv is
        port( mclk : in std_logic;
              clr : in std_logic;
              clk190: out std_logic;
              clk48: out std_logic
            );
    end component;

    component mod10kcnt is
        port( clr : in STD_LOGIC;
              clk : in STD_LOGIC;
              start : in std_logic;
              pause : in std_logic;
              q : out STD_LOGIC_VECTOR(13 downto 0)
            );
    end component;

    component binBCD14 is
        Port ( b : in STD_LOGIC_VECTOR(13 downto 0);
              p : out STD_LOGIC_VECTOR(16 downto 0));
    end component;

    component x7segbc is
        port( x : in std_logic_vector(15 downto 0);
              cclk : in std_logic;
              clr : in std_logic;
              a_to_g : out std_logic_vector(6 downto 0);
              an : out std_logic_vector(3 downto 0);
              dp : out std_logic
            );
    end component;

```

```

signal b : std_logic_vector(13 downto 0);
signal p : std_logic_vector(16 downto 0);
signal clr, start, pause, clk48, clk190 : std_logic;

begin
clr <= btn(0);
pause <= btn(1);
start <= btn(2);

u1: clkdiv port map(
    mclk => mclk,
    clr => clr,
    clk190 => clk190,
    clk48 => clk48
);
u2: mod10kcnt port map(
    clr => clr,
    start => start,
    pause => pause,
    clk => clk48,
    q => b
);
u3: binBCD14 port map(
    b => b,
    p => p
);
);
u4: x7segbc port map(
    x => p(15 downto 0),
    cclk => clk190,
    clr => clr,
    a_to_g => a_to_g,
    an => an,
    dp => dp
);
end Behavioral;

```


Pendefinisian Pin

```


1 NET btn(0) LOC = M13;
2 NET btn(1) LOC = M14;
3 NET btn(2) LOC = L13;
4
5 NET a_to_g(0) LOC = N16;
6 NET a_to_g(1) LOC = F13;
7 NET a_to_g(2) LOC = R16;
8 NET a_to_g(3) LOC = P15;
9 NET a_to_g(4) LOC = N15;
10 NET a_to_g(5) LOC = G13;
11 NET a_to_g(6) LOC = E14;
12
13 NET an(0) LOC = D14;
14 NET an(1) LOC = G14;
15 NET an(2) LOC = F14;
16 NET an(3) LOC = E13;
17
18 NET dp LOC = P16;

```


RTL Skematik

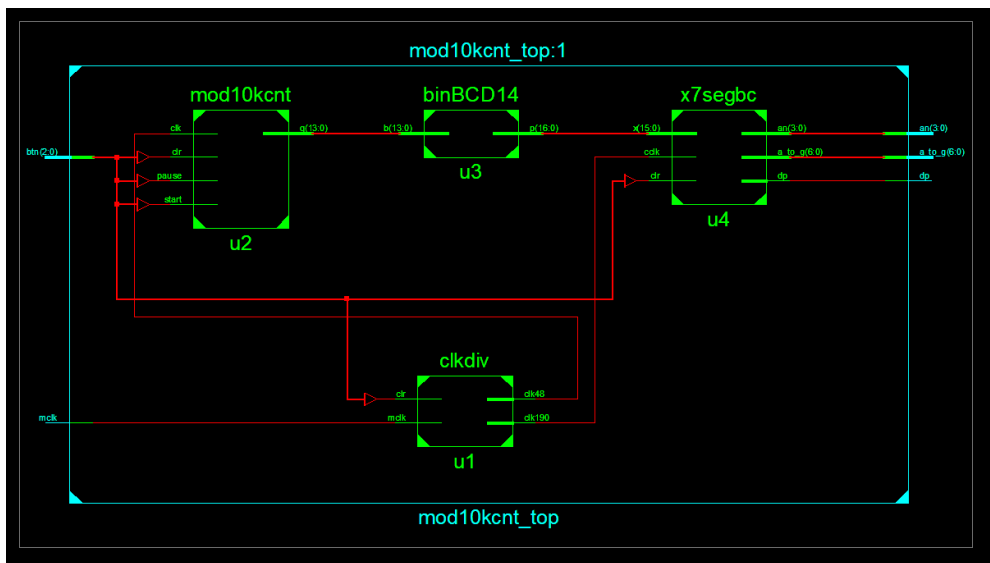

Hasil Pada FPGA Board

 

Gambar pada stopwatch sedang di mulai



Gambar pada stopwatch sedang di pause



Gambar pada stopwatch sedang di reset

7. Analisa

		Nilai
		Date
<input type="checkbox"/>	Analisa dan kesimpulan	
<input type="checkbox"/>		
<input type="checkbox"/>	→ Langkah Percobaan	
<input type="checkbox"/>	Pada praktikum tersebut, merupakan program rangkaian Counter. Rangkaian tersebut	
<input type="checkbox"/>	menampilkan output desimal mulai dari 0 hingga limit program yang telah disetting. Pada	
<input type="checkbox"/>	percobaan menggunakan Counter mod 10, dimana program tersebut akan menampilkan	
<input type="checkbox"/>	cirika mulai dari 0 hingga 9 dan kembali lagi mulai 0. Selanjutnya percobaan tersebut	
<input type="checkbox"/>	menampilkan cirika hingga 9999. Setelah cirika tersebut tampil, program akan	
<input type="checkbox"/>	reset kembali dan menampilkan ulang mulai dari 0. Agar Counter dapat bekerja dibantu	
<input type="checkbox"/>	sebuah clock. Pada program tersebut clock berasal dari clock desier dengan frekuensi	
<input type="checkbox"/>	48 Hz dan 190 Hz. Lalu output di lanjutkan ke BCD converter dan dilanjutkan	
<input type="checkbox"/>	pada 7 segment display decoder sebagai output akhir.	
<input type="checkbox"/>	→ Mini Project	
<input type="checkbox"/>	Pada program kali ini merupakan program yang menampilkan output layaknya	
<input type="checkbox"/>	sebuah stopwatch, dimana terdapat button sebagai start, stop, dan reset. Untuk	
<input type="checkbox"/>	strukturnya terdapat program mod 10 / counter, clock, Biner to BCD dan 7 seg	
<input type="checkbox"/>	decoder. Pada bagian arsitektur telah disetting input yang berasal dari button agar	
<input type="checkbox"/>	counter dapat start, pause dan reset.	