

# 1 D4 - TEKKOM B

## DECODER 7 SEGMENT

### PART 2



Nama	:	Septian Bagus Jumentoro
Kelas	:	1 – D4 Teknik Komputer B
NRP	:	3221600039
Dosen	:	Reni Soelistijorini B.Eng., MT.
Mata Kuliah	:	Praktikum Rangkaian Logika 2
Hari/Tgl. Praktikum	:	Jumat, 13 Mei 2022


## Percobaan 7 – Decoder 7 Segmen

### 1. Tujuan

- Mampu mengimplementasikan algoritma decoder 7 segmen.
- Dapat menampilkan nilai masukan keluaran pada 7 segmen dalam modul FPGA.

## 2. Teori

Pada percobaan ini akan mempelajari beberapa rangkaian kombinasional yaitu BCD to 7'segmen. Rangkaian BCD to 7'segmen adalah rangkaian kombinasional yang mengkodekan bilangan biner menjadi bilangan desimal, selanjutnya bilangan tersebut di konfigurasi menjadi tampilan seven segmen. Konfigurasi seven segmen pada board spartan 3 ditunjukkan pada gambar 7.1.

 

Gambar 7. 1 Konfigurasi seven segmen pada board spartan3

Terdapat 4 buah sevensegmen yang disusun secara pararel dengan data 1-g dan dot di rangkai menjadi satu. Sedangkan kendali tampilan di atur melalui pin AN di setiap segmen.

## 3. Alat dan Bahan

1. PC yang sudah terinstall ISE 13.1
2. Xilinx Sparatan 3
3. Downloader JTAG USB
4. Power Supply 5 volt

## 4. Langkah Percobaan

### A. 7 Segmen Display.

Percobaan ini akan membuat program dengan masukan switch dan keluaran 7segmen.

1. Buatlah new project dengan nama Lab7A.
2. Tambahkan program dibawah ini.
  - a. 7-segmen Decoder dengan Logic Equation

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity hex7seg is
    Port ( x : in  STD_LOGIC_VECTOR (3 downto 0);
          a_to_g : out  STD_LOGIC_VECTOR (6 downto 0));
end hex7seg;
architecture hex7seg_1e of hex7seg is
begin
    a_to_g(6) <= (not x(3) and not x(2) and not x(1) and x(0)) -- a
               or (not x(3) and x(2) and not x(1) and not x(0))
               or ( x(3) and x(2) and not x(1) and x(0))
               or ( x(3) and not x(2) and x(1) and x(0));
    a_to_g(5) <= (x(2) and x(1) and not x(0)) -- b
               or ( x(3) and x(1) and x(0))
               or (not x(3) and x(2) and not x(1) and x(0))
               or ( x(3) and x(2) and not x(1) and not x(0));
    a_to_g(4) <= (not x(3) and not x(2) and x(1) and not x(0)) -- c
               or (x(3) and x(2) and x(1))
               or (x(3) and x(2) and not x(0));
    a_to_g(3) <= (not x(3) and not x(2) and not x(1) and x(0)) -- d
               or (not x(3) and x(2) and not x(1) and not x(0))
               or (x(3) and not x(2) and x(1) and not x(0))
               or (x(2) and x(1) and x(0));
    a_to_g(2) <= (not x(3) and x(0)) -- e
               or (not x(3) and x(2) and not x(1))
               or (not x(2) and not x(1) and x(0));
    a_to_g(1) <= (not x(3) and not x(2) and x(0)) -- f
               or (not x(3) and not x(2) and x(1))
               or (not x(3) and x(1) and x(0))
               or (x(3) and x(2) and not x(1) and x(0));
    a_to_g(0) <= (not x(3) and not x(2) and not x(1)) -- g
               or (x(3) and x(2) and not x(1) and not x(0))
               or (not x(3) and x(2) and x(1) and x(0));
end hex7seg_1e;

```

b. 7-Segmen Decoder Case Statement

```

begin
  process(x)
  begin
    case x is
      -- abcdefg
      when x"0" => a_to_g <= "0000001"; -- 0
      when x"1" => a_to_g <= "1001111"; -- 1
      when x"2" => a_to_g <= "0010010"; -- 2
      when x"3" => a_to_g <= "0000110"; -- 3
      when x"4" => a_to_g <= "1001100"; -- 4
      when x"5" => a_to_g <= "0100100"; -- 5
      when x"6" => a_to_g <= "0100000"; -- 6

      when x"7" => a_to_g <= "0001111"; -- 7
      when x"8" => a_to_g <= "0000000"; -- 8
      when x"9" => a_to_g <= "0000100"; -- 9
      when x"A" => a_to_g <= "0001000"; -- a
      when x"B" => a_to_g <= "1100000"; -- b
      when x"C" => a_to_g <= "0110001"; -- c
      when x"D" => a_to_g <= "1000010"; -- d
      when x"E" => a_to_g <= "0110000"; -- e
      when others => a_to_g <= "0111000"; -- f

    end case;
  end process;
end hex7segb;

```

Script 7. 2. 7-Segmen Case Statement

### c. 7-Segmen Top Level

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity hex7seg_top is
  Port ( sw : in  STD_LOGIC_VECTOR (3 downto 0);
        a_to_g : out  STD_LOGIC_VECTOR (6 downto 0);
        an : out  STD_LOGIC_VECTOR (3 downto 0);
        dp : out  STD_LOGIC );
end hex7seg_top;


architecture hex7seg_top of hex7seg_top is
  component hex7segb is
    port(
      x: in STD_LOGIC_VECTOR (3 downto 0);
      a_to_g : out  STD_LOGIC_VECTOR (6 downto 0)
    );
  end component;
begin
  an <= "0000"; -- all digit on
  dp <= '1'; -- dp off
  d4: hex7seg port map (x=>sw, a_to_g=>a_to_g);

end hex7seg_top;

```

Script 7. 3. 7-Segmen Top Level


3. Atur agar program hex7seg\_top menjadi Top modul.
4. Lakukan Synthesizes-XST, pastikan tidak ada error.
5. Tambahkan konfigurasi pin dengan cara tambahkan new source| Implementation Constraints File. Beri nama hex7seg\_top.

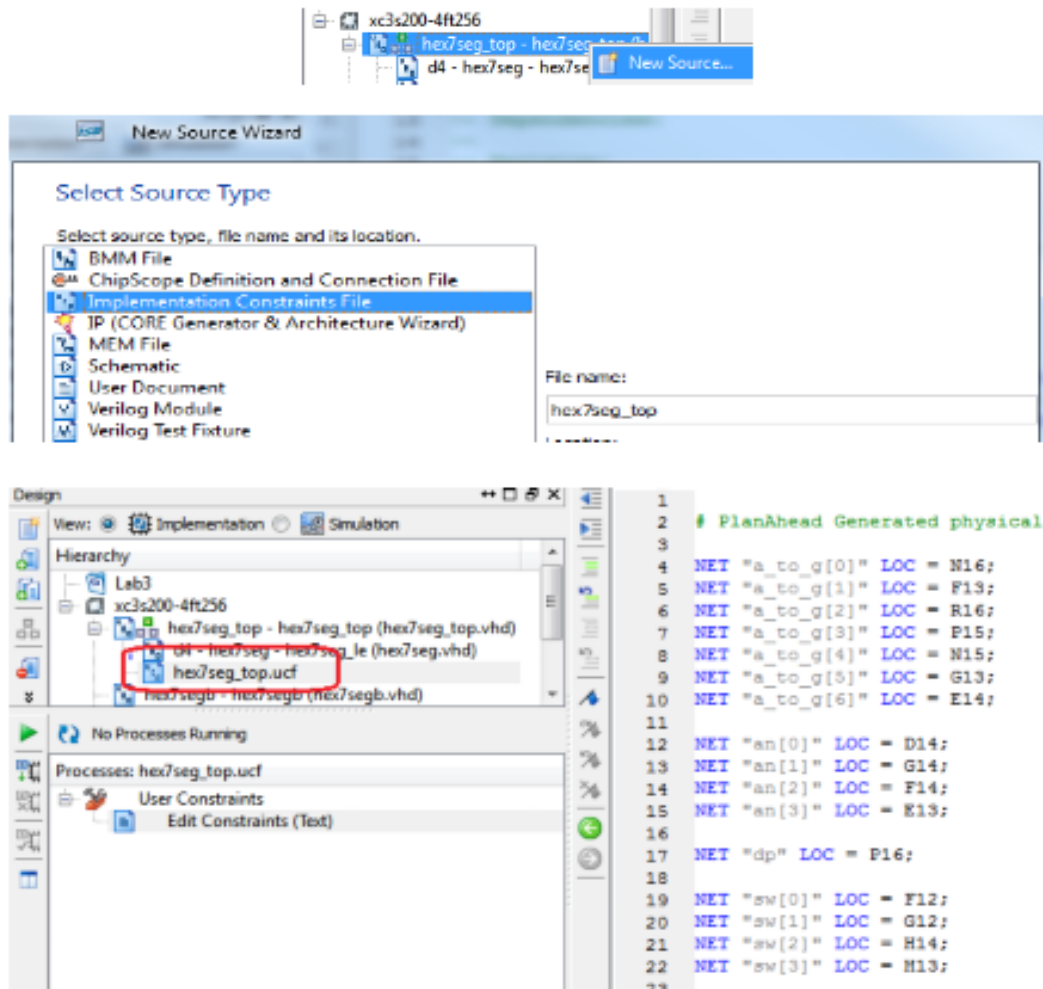

6. Klik Pada jendela hex7seg\_top.ucf dan isikan konfigurasi pin seperti gambar diatas.
7. Lakukan SynthesizesXST | Implement Design | Generate programming File sampai dengan programming ke board Spartan-3 FPGA.
8. Atur switch sesuai dengan 1 digit angka terakhir nrp anda.
9. Foto hasil tampilan seven segmen.


## B. Multiplexing 7-Segmen

Percobaan ini untuk menampilkan data angka “1234” ke 7segmen dengan pengaturan tampilan dari enable 7segmen melalui push botton. Blok program ditunjukkan pada gambar 7.2.

 

Gambar 7. 2 Blok program mux7seg

 1. Buatlah new project dengan nama Lab7B.
2. Tambahkan Program baru dengan nama mux7seg\_top.
3. Pastikan top modul pada mux7seg\_top.vhd.



4. Tulis program mux7seg\_top.vhd berikut ini.

```
library IEEE;
use IEEE.STD_LOGIC_C_VECTOR.ALL;

entity mux7seg_top is
    Port ( btn : in  STD_LOGIC_VECTOR (3 downto 0);
          a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
          an : out  STD_LOGIC_VECTOR (3 downto 0);
          dp : out  STD_LOGIC );
end mux7seg_top;

architecture mux7seg of mux7seg_top is
    signal x : STD_LOGIC_VECTOR (15 downto 0);
    signal s : STD_LOGIC_VECTOR (1 downto 0);
    signal digit : STD_LOGIC_VECTOR (3 downto 0);
```

```
begin

    x <= x"1234";
    an <= not btn;
    s(1) <= btn(2) or btn(3);
    s(0) <= btn(1) or btn(3);
    dp <= '1';

    -- quad 4 to 1 mux: mux44
    process(s)
    begin
        case s is
            when "00" => digit <= x(3 downto 0);
            when "01" => digit <= x(7 downto 4);
```

```


        when "10" => digit <= x(11 downto 8);
        when others => digit <= x(15 downto 12);
    end case;
end process;

process(digit)
begin
    case digit is
        -- abcdefg
        when x"0" => a_to_g <= "0000001"; --0
        when x"1" => a_to_g <= "1001111"; --1
        when x"2" => a_to_g <= "0010010"; --2
        when x"3" => a_to_g <= "0000110"; --3
        when x"4" => a_to_g <= "1001100"; --4
        when x"5" => a_to_g <= "0100100"; --5
        when x"6" => a_to_g <= "0100000"; --6
        when x"7" => a_to_g <= "0001111"; --7
        when x"8" => a_to_g <= "0000000"; --8
        when x"9" => a_to_g <= "0000100"; --9
        when x"A" => a_to_g <= "0001000"; --a
        when x"B" => a_to_g <= "1100000"; --b
        when x"C" => a_to_g <= "0110001"; --c
        when x"D" => a_to_g <= "1000010"; --d
        when x"E" => a_to_g <= "0110000"; --e
        when others => a_to_g <= "0111000"; --f
    end case;
end process;
end mux7seg;

```

*Program 4. Multiplexing 7-Segmen*

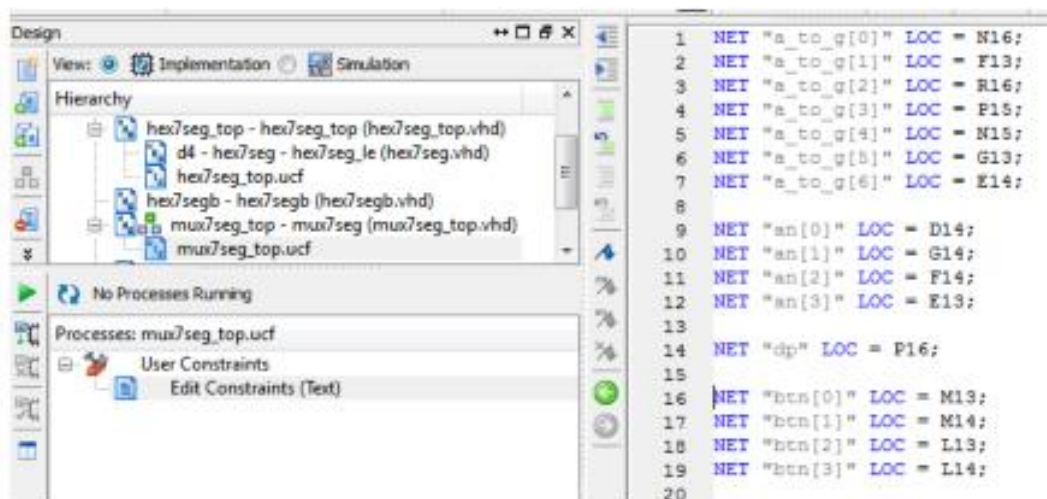5. Tambahkan file .ucf untuk konfigurasi pin. Seperti dibawah ini.




6. Jalankan programnya dan upload program ke dalam chip FPGA-nya
7. Ubah program agar tampilkan di seven segmen adalah 4 digit terakhir NRP anda.
8. Fotokan hasil tampilannya.

### C. Multiplexing 7segment Display dengan ClockDivider

Tampilan dari empat 7segment akan diatur secara otomatis oleh ClockDivider.

Ada 2 model program yang akan ditampilkan yaitu **x7seg** dan **x7segb**.

 

Gambar 7. 3. Blok program x7seg  
lxxxix

x7seg.

1. Buatlah **new project** dengan nama **Lab7C1**.
2. Tambahkan program dibawah ini.
3. Seperti pada langkah sebelumnya. Tambahkan program vhdl berikut ini.



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity x7seg is
    Port ( x : in  STD_LOGIC_VECTOR (15 downto 0);
          clk : in  STD_LOGIC;
          clr : in  STD_LOGIC;
          a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
          an : out  STD_LOGIC_VECTOR (3 downto 0);
          dp : out  STD_LOGIC);
end x7seg;

architecture x7seg of x7seg is
    signal s : STD_LOGIC_VECTOR (1 downto 0);
    signal digit : STD_LOGIC_VECTOR (3 downto 0);
    signal aen : STD_LOGIC_VECTOR (3 downto 0);
    signal clkdiv : STD_LOGIC_VECTOR (20 downto 0);
begin
    s <= clkdiv(20 downto 19);
    aen <= "1111";
    dp <= '1';
    -- Quad 4 to 1 mux
    process(s,x)
    begin
        case s is
            when "00" => digit <= x(3 downto 0);
            when "01" => digit <= x(7 downto 4);
            when "10" => digit <= x(11 downto 8);
            when others => digit <= x(15 downto 12);
        end case;
    end process;

    -- 7-segment decoder: hex7seg
    process(digit)
    begin
        case digit is
            when x"0" => a_to_g <= "0000001"; -- 0
            when x"1" => a_to_g <= "1001111"; -- 1
            when x"2" => a_to_g <= "0010010"; -- 2

```

```

        when x"3" => a_to_g <= "0000110"; -- 3
        when x"4" => a_to_g <= "1001100"; -- 4
        when x"5" => a_to_g <= "0100100"; -- 5
        when x"6" => a_to_g <= "0100000"; -- 6
    when x"7" => a_to_g <= "0001111"; -- 7
        when x"8" => a_to_g <= "0000000"; -- 8
        when x"9" => a_to_g <= "0000100"; -- 9
        when x"A" => a_to_g <= "0001000"; -- a
        when x"B" => a_to_g <= "1100000"; -- b
        when x"C" => a_to_g <= "0110001"; -- c
        when x"D" => a_to_g <= "1000010"; -- d
        when x"E" => a_to_g <= "0110000"; -- e
        when others => a_to_g <= "0111000"; -- f
    end case;
end process;

-- Digit select: ancode
process(s,aen)
begin
    an <= "1111";
    if aen(conv_integer(s))='1' then
        an(conv_integer(s))<='0';
    end if;
end process;

-- Clock divider
process(clk, clr)
begin
    if clr='1' then
        clkdiv <= (others => '0');
    elsif clk'event and clk='1' then
        clkdiv <= clkdiv+1;
    end if;
end process;

end x7seg;

```

*Program 5. Multiplexing 7-Segmen dengan ClockDivider A*

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity x7seg_top is
    Port ( mclk : in STD_LOGIC; xci
          btn : in STD_LOGIC;

```

```

        a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
        an : out STD_LOGIC_VECTOR (3 downto 0);
        dp : out STD_LOGIC;
    end x7seg_top;

    architecture x7seg_top of x7seg_top is
        component x7seg is
            Port ( x : in STD_LOGIC_VECTOR (15 downto 0);
                  clk : in STD_LOGIC;
                  clr : in STD_LOGIC;
                  a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
                  an : out STD_LOGIC_VECTOR (3 downto 0);
                  dp : out STD_LOGIC );
        end component;
        signal x: STD_LOGIC_VECTOR (15 downto 0);
    begin
        x <= x"1234";
        x1 : x7seg port map
            (x=>x, clk=>clk, clr=>btn, a_to_g=>a_to_g, an=>an, dp=>dp);
    end x7seg_top;

```

Program 6. Multiplexing 7-Segmen Top Modul

4. Jalankan programnya dan upload program ke dalam chip FPGA-nya
5. Ubah program agar tampilkan di seven segmen adalah "Kelas(A/B)" - "0" - 2 digit terakhir NRP anda.
6. Fotokan hasil tampilannya.

x7segb.

1. Buatlah **new project** dengan nama **Lab7C2**.
2. Tambahkan program dibawah ini.
3. Seperti pada langkah sebelumnya. Tambahkan program vhd berikut ini.

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

xcii

```

entity x7segb is
    Port ( x : in  STD_LOGIC_VECTOR (15 downto 0);
          clk : in  STD_LOGIC;
          clr : in  STD_LOGIC;
          a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
          an : out  STD_LOGIC_VECTOR (3 downto 0);
          dp : out  STD_LOGIC);
end x7segb;

architecture x7seg of x7segb is
    signal s : STD_LOGIC_VECTOR (1 downto 0);
    signal digit : STD_LOGIC_VECTOR (3 downto 0);
    signal aen : STD_LOGIC_VECTOR (3 downto 0);
    signal clkdiv : STD_LOGIC_VECTOR (20 downto 0);

begin
    s <= clkdiv(20 downto 19);
    dp <= '1';

    -- set aen(3 downto 0) for leading blanks
    aen(3) <= x(15) or x(14) or x(13) or x(12);
    aen(2) <= x(15) or x(14) or x(13) or x(12) or
              x(11) or x(10) or x(9) or x(8);
    aen(1) <= x(15) or x(14) or x(13) or x(12) or
              x(11) or x(10) or x(9) or x(8) or
              x(7) or x(6) or x(5) or x(4);
    aen(0) <= '1'; -- digit 0 always on

    -- Quad 4 to 1 mux
    process(s,x)
    begin
        case s is
            when "00" => digit <= x(3 downto 0);
            when "01" => digit <= x(7 downto 4);
            when "10" => digit <= x(11 downto 8);
            when others => digit <= x(15 downto 12);
        end case;
    end process;

    -- 7-segment decoder: hex7seg
    process(digit)
    begin
        case digit is
            when x"0" => a_to_g <= "0000001"; -- 0
            when x"1" => a_to_g <= "1001111"; -- 1
            when x"2" => a_to_g <= "0010010"; -- 2

```

```

        when x"3" => a_to_g <= "0000110"; --3
        when x"4" => a_to_g <= "1001100"; --4
        when x"5" => a_to_g <= "0100100"; --5
        when x"6" => a_to_g <= "0100000"; --6
        when x"7" => a_to_g <= "0001111"; --7
        when x"8" => a_to_g <= "0000000"; --8
        when x"9" => a_to_g <= "0000100"; --9
        when x"A" => a_to_g <= "0001000"; --a
        when x"B" => a_to_g <= "1100000"; --b
        when x"C" => a_to_g <= "0110001"; --c
        when x"D" => a_to_g <= "1000010"; --d
        when x"E" => a_to_g <= "0110000"; --e
        when others => a_to_g <= "0111000"; --f

        end case;
    end process;

-- Digit select: ancode
    process(s, aen)
    begin
        an <= "1111";
        if aen(conv_integer(s)) = '1' then
            an(conv_integer(s)) <= '0';
        end if;
    end process;

-- Clock Divider
    process(clk, clr)
    begin
        if clr = '1' then
            clkdiv <= (others => '0');
        elsif clk'event and clk = '1' then
            clkdiv <= clkdiv + 1;
        end if;
    end process;
end x7seg;

```

Program 7. Multiplexing 7-Segmen dengan ClockDivider B

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity x7segb_top is
    Port ( clk : in STD_LOGIC;
          btn : in STD_LOGIC_VECTOR (3 downto 0);
          sw : in STD_LOGIC_VECTOR (7 downto 0);
          a_to_g : out STD_LOGIC_VECTOR (6 downto 0);

```

```

          an : out STD_LOGIC_VECTOR (3 downto 0);
          dp : out STD_LOGIC);
end x7segb_top;

architecture x7seg_top of x7segb_top is
    component x7segb is
        Port ( x : in STD_LOGIC_VECTOR (15 downto 0);
              clk : in STD_LOGIC;
              clr : in STD_LOGIC;
              a_to_g : out STD_LOGIC_VECTOR (6 downto 0);
              an : out STD_LOGIC_VECTOR (3 downto 0);
              dp : out STD_LOGIC);
    end component;

    signal x : STD_LOGIC_VECTOR (15 downto 0);
begin
    -- concatenate switch and 3 buttons
    x <= sw & btn(2 downto 0) & "01010"; -- digit 0 =A
    x2 : x7segb port map
        (x=>x, clk=>clk, clr=>btn(3), a_to_g=>a_to_g, an=>an,
        dp=>dp);
end x7seg_top;

```

Program 8. Multiplexing 7-Segmen Top Modul B

4. Jalankan programnya dan upload program ke dalam chip FPGA-nya
5. Ubah program agar tampilan di seven segmen adalah “CE” – 2 digit terakhir NRP anda.
6. Fotokan hasil tampilan seven segmen dan konfigurasi switch.

## 5. Hasil Percobaan

### Percobaan C - A

#### Definisi Pin

```
1 NET "mclk" CLOCK_DEDICATED_ROUTE = FALSE;  
2 NET btn LOC = M13;  
3  
4 NET y(0) LOC = N16;  
5 NET y(1) LOC = F13;  
6 NET y(2) LOC = R16;  
7 NET y(3) LOC = P15;  
8 NET y(4) LOC = N15;  
9 NET y(5) LOC = G13;  
10 NET y(6) LOC = E14;  
11  
12 NET an(0) LOC = D14;  
13 NET an(1) LOC = G14;  
14 NET an(2) LOC = F14;  
15 NET an(3) LOC = E13;  
16  
17 NET dp LOC = P16;
```

#### Tampilan Pada Board



Tampilan b039 pada 7 segment display

## Percobaan C - B

### Definisi Pin

```
1 NET "clk" CLOCK_DEDICATED_ROUTE = FALSE;
2
3 NET btn(0) LOC = M13;
4 NET btn(1) LOC = M14;
5 NET btn(2) LOC = L13;
6 NET btn(3) LOC = L14;
7
8 NET sw(0) LOC=F12;
9 NET sw(1) LOC=G12;
10 NET sw(2) LOC=H14;
11 NET sw(3) LOC=H13;
12 NET sw(4) LOC=J14;
13 NET sw(5) LOC=J13;
14 NET sw(6) LOC=K14;
15 NET sw(7) LOC=K13;
16
17 NET y(0) LOC = N16;
18 NET y(1) LOC = F13;
19 NET y(2) LOC = R16;
20 NET y(3) LOC = P15;
21 NET y(4) LOC = N15;
22 NET y(5) LOC = G13;
23 NET y(6) LOC = E14;
24
25 NET an(0) LOC = D14;
26 NET an(1) LOC = G14;
27 NET an(2) LOC = F14;
28 NET an(3) LOC = E13;
29
30 NET dp LOC = P16;
```

### Tampilan pada Board



Tampilan CE39 pada 7 segment display

## Mini Project

### Source Code Binary to BCD

```
--
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.std_logic_unsigned.all;|
23
24 entity projectA_bcd is
25 port( b : in STD_LOGIC_VECTOR(7 downto 0);
26       p : out STD_LOGIC_VECTOR(9 downto 0)
27       );
28 end projectA_bcd;
29
30 architecture Behavioral of projectA_bcd is
31 begin
32     bcd1:process(b)
33     variable z :STD_LOGIC_VECTOR(17 downto 0);
34
35     begin
36         for i in 0 to 17 loop
37             z(i):= '0' ;
38         end loop;
39
40         z(10 downto 3):=b;
41         for i in 0 to 4 loop
42             if z(11 downto 8)> 4 then
43                 z(11 downto 8):= z(11 downto 8)+3;
44             end if;
45             if z(15 downto 12)>4 then
46                 z(15 downto 12):= z(15 downto 12)+3;
47             end if;
48
49             z(17 downto 1):= z(16 downto 0);
50         end loop;
51
52         p <= z(17 downto 8);
53     end process bcd1;
54
55 end Behavioral;
56
57
```

### Source Code 7 Segment Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
entity projectA is
port( x : in STD_LOGIC_VECTOR(15 downto 0);
      clk : in STD_LOGIC;
      clr : in STD_LOGIC;
      y : out STD_LOGIC_VECTOR(6 downto 0);
      an : out STD_LOGIC_VECTOR(3 downto 0);
      dp : out STD_LOGIC);
end projectA;
architecture Behavioral of projectA is
    signal s : STD_LOGIC_VECTOR(1 downto 0);
    signal digit : STD_LOGIC_VECTOR(3 downto 0);
    signal aen : STD_LOGIC_VECTOR(3 downto 0);
    signal clkdiv : STD_LOGIC_VECTOR(20 downto 0);
begin
    s <= clkdiv(20 downto 19);
    aen <= "1111";
    dp <= '1';
    process(s,x)
    begin
        case s is
            when "00" => digit <= x(3 downto 0);
            when "01" => digit <= x(7 downto 4);
            when "10" => digit <= x(11 downto 8);
            when others => digit <= x(15 downto 12);
        end case;
    end process;
end projectA;
```



```

process(digit)
begin
    case digit is
        when x"0" => y <= "0000001";
        when x"1" => y <= "1001111";
        when x"2" => y <= "0010010";
        when x"3" => y <= "0000110";
        when x"4" => y <= "1001100";
        when x"5" => y <= "0100100";
        when x"6" => y <= "0100000";
        when x"7" => y <= "0001111";
        when x"8" => y <= "0000000";
        when others => y <= "0000100";
    end case;
end process;
process(s,aen)
begin
    an <= "1111";
    if aen(conv_integer(s)) = '1' then
        an(conv_integer(s)) <= '0';
    end if;
end process;
process(clk,clr)
begin
    if clr = '1' then
        clkdiv <= (others => '0');
    elsif clk' event and clk = '1' then
        clkdiv <= clkdiv+1;
    end if;
end process;
end Behavioral;

```

## Top Modul

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity projectA_top is
port( clk : in STD_LOGIC;
      btn : in STD_LOGIC;
      sw : in STD_LOGIC_VECTOR(7 downto 0);
      y : out STD_LOGIC_VECTOR(6 downto 0);
      an : out STD_LOGIC_VECTOR(3 downto 0);
      dp : out STD_LOGIC
    );
end projectA_top;

architecture Behavioral of projectA_top is
    component projectA is
        port( x : in STD_LOGIC_VECTOR(15 downto 0);
              clk : in STD_LOGIC;
              clr : in STD_LOGIC;
              y : out STD_LOGIC_VECTOR(6 downto 0);
              an : out STD_LOGIC_VECTOR(3 downto 0);
              dp : out STD_LOGIC
            );
    end component;
end Behavioral;

```

```

component projectA_bcd is

    port(
        b : in STD_LOGIC_VECTOR(7 downto 0);

        p : out STD_LOGIC_VECTOR(9 downto 0)

    );

end component;

signal x: STD_LOGIC_VECTOR(15 downto 0);
signal adder : STD_LOGIC_VECTOR(7 downto 0);
signal bcd : STD_LOGIC_VECTOR(9 downto 0);

begin

    adder <= bcd(7 downto 0)+1;
    x <= bcd(7 downto 0) & adder;

    x1 :projectA port map( x => x,

                                clk => clk,
                                clr => btn,

```

## Definisi Pin

```

1  NET sw(0) LOC = F12;
2  NET sw(1) LOC = G12;
3  NET sw(2) LOC = H14;
4  NET sw(3) LOC = H13;
5  NET sw(4) LOC = J14;
6  NET sw(5) LOC = J13;
7  NET sw(6) LOC = K14;
8  NET sw(7) LOC = K13;
9
10 NET btn LOC = M13;
11
12 NET y(0) LOC = N16;
13 NET y(1) LOC = F13;
14 NET y(2) LOC = R16;
15 NET y(3) LOC = P15;
16 NET y(4) LOC = N15;
17 NET y(5) LOC = G13;
18 NET y(6) LOC = E14;
19
20 NET an(0) LOC = D14;
21 NET an(1) LOC = G14;
22 NET an(2) LOC = F14;
23 NET an(3) LOC = E13;
24
25 NET dp LOC = P16;

```

Tampilan pada Board



2 digit paling kiri berasal dari input Biner Switch.  
2 digit dari kanan merupakan nilai dari switch  
dengan +1



2 digit paling kiri berasal dari input Biner Switch.  
2 digit dari kanan merupakan nilai dari switch  
dengan +1

## 6. Analisa dan Kesimpulan

No. \_\_\_\_\_

Date: \_\_\_\_\_

☐ Analisa dan kesimpulan

☐

☐ → Percobaan C - a

☐ Pada praktikum tersebut merupakan program rangkaian Decoder 7 segment dengan tambahan rangkaian 16 to 1 mux dan clock divider. Rangkaian ini hampir sama dengan percobaan B, hanya saja digit select berguna untuk kedip sesuai frekuensi.

☐ → Percobaan C - b

☐ Pada praktikum tersebut hampir sama dengan percobaan sebelumnya, hanya berbeda input. Inputnya sendiri ada 4 untuk mengubah digit paling kanan dan 4 untuk mengubah digit paling kiri. Untuk mengubah digit terakhir dapat langsung mengubah source code pada Top Modul.

☐ → Mini project

☐ Pada praktikum tersebut merupakan gabungan dari Decode 7 segment, Binary to BCD dan Top Modul. Pada program tersebut memerlukan 4 input bit yang bernilai biner. Dari nilai biner diubah menjadi BCD. Lalu hasil dari konversi tersebut dimasukkan ke Decoder 7 segment untuk diaktifkan output pada 7 segment display.

☐

☐

☐